

# Thevenin and Norton Equivalents

Michael Brodskiy

Professor: N. Sun

February 1, 2023

- Circuit Equivalence
  - If there are two circuits, and the same voltage,  $v_a$  is applied to both, if  $I_A = I_B$  then the circuits are considered equivalent
  - Same thing for same current applied and same voltage output
- Resistor Equivalence
  - Resistors can be connected in circuits like a delta connection
  - As well as a Y connection
  - A delta connection can be transformed into a Y connection and vice versa using transformation technique
  - This will often help in circuits
- Transformations can be established from one to the other, as shown in Figure 1, using the following

$$\boxed{R_1 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_c R_a}{R_a + R_b + R_c}, \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}}$$

$$\boxed{R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}, \quad R_2 = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}, \quad R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}}$$

- A voltage source with a series resistor can be transformed into a current source with a resistor in parallel, as shown in Figure 2
- A parallel resistor with a voltage source can be removed (replaced by an open) for transformation, as shown in Figure 3
- A series resistor with a current source can be removed (replaced by a short) for transformation, as shown in Figure 4

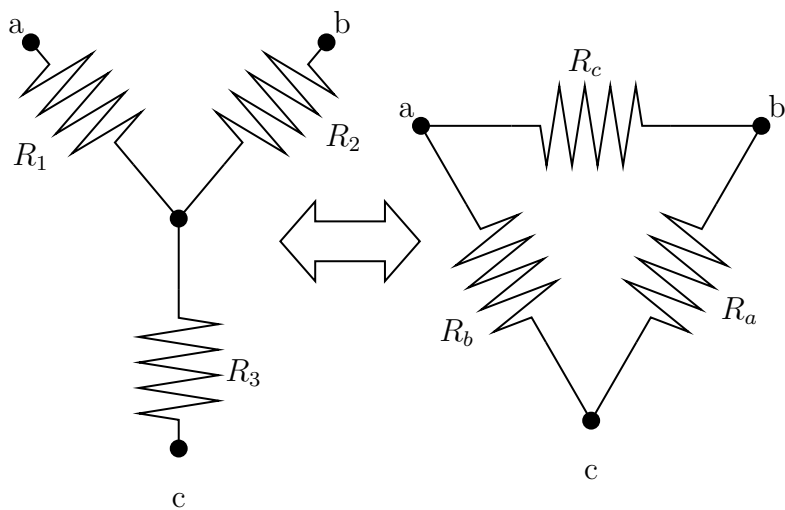


Figure 1: Delta and Y Circuit Configurations

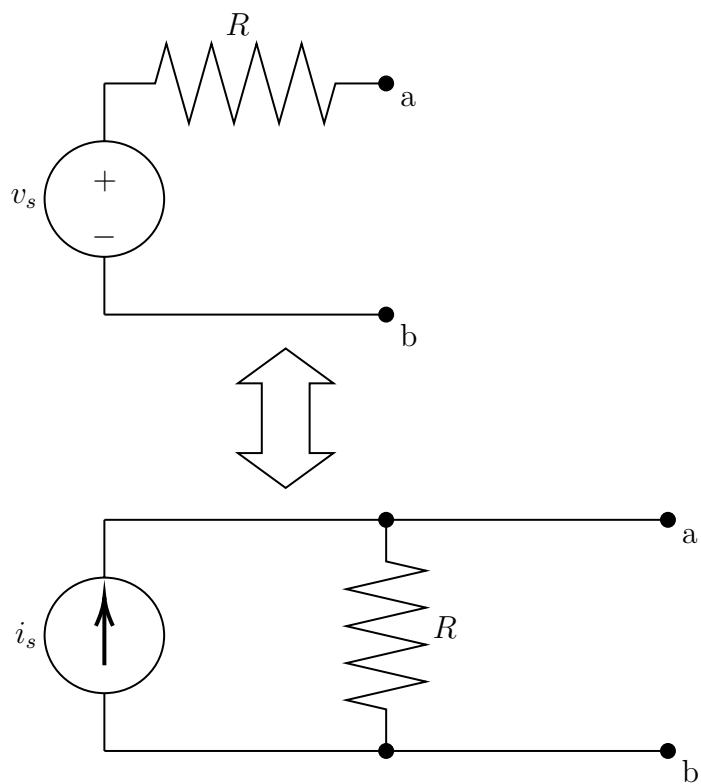


Figure 2: Converting Between Voltage and Current

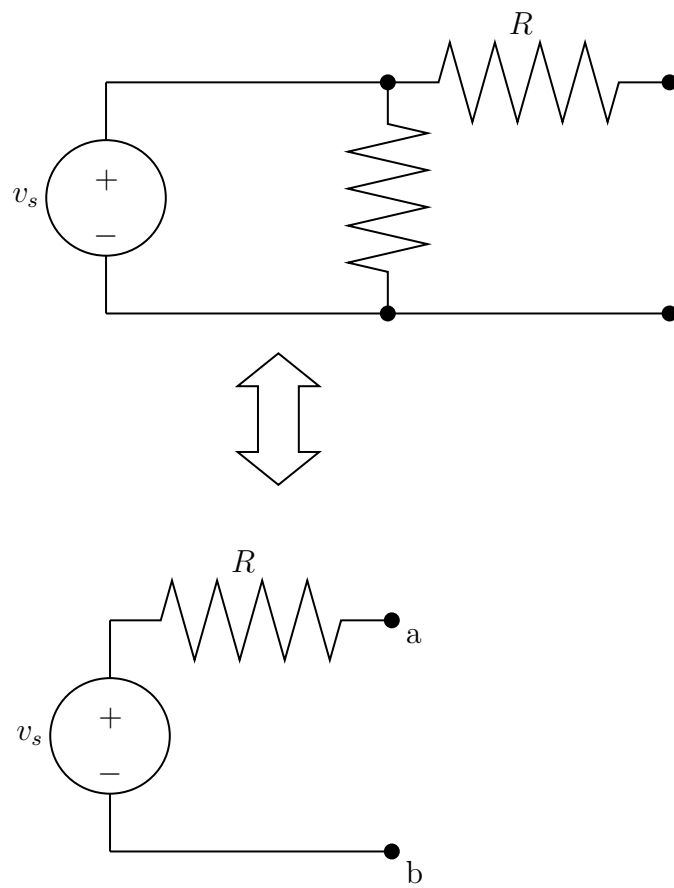


Figure 3: Converting Voltage Sources

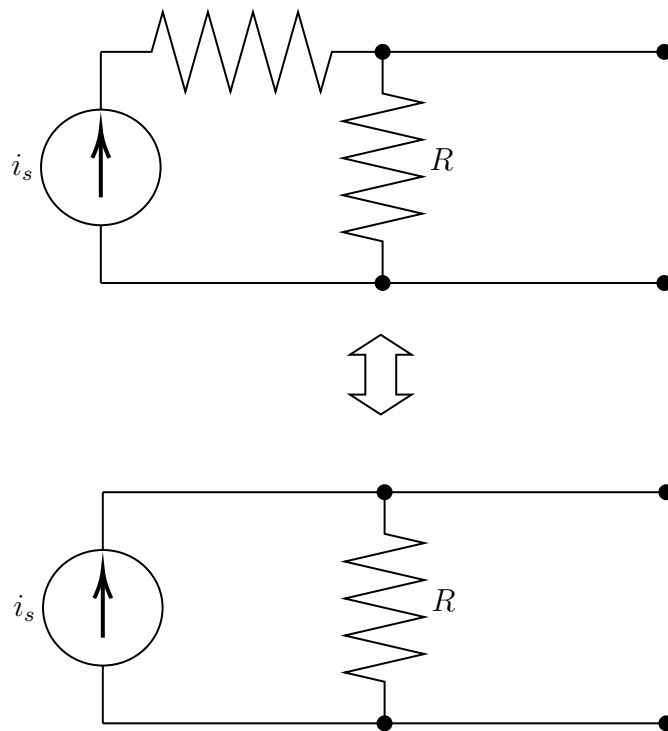


Figure 4: Converting Current Sources

- Some systems may be very complex, but we may be only interested in how it behaves at two terminals
  - Actual circuit can be converted into an equivalent circuit, called Thevenin equivalent
  - It essentially replaces the actual circuit with a voltage source with a series resistor
  - The voltage source is called the Thevenin voltage  $V_{TH}$
  - The equivalent input resistance is called the Thevenin resistor  $R_{TH}$
- Thevenin Equivalence is a two-step process:
  1. Analyze the circuit and find the open circuit voltage  $v_{oc}$
  2. Analyze the circuit and find the short circuit current across the terminal  $i_{sc}$ 
    - Some circuits only work properly over a certain range of loads (not with  $R_L = 0$ , for example)
    - For this type of circuit, to determine  $R_{TH}$  use an acceptable  $R_L$  and compute  $R_{TH}$  by using the voltage divider equation shown below

$$V_{RL} = V_{TH} \frac{R_L}{R_{TH} + R_L}$$

- Note that only the process of determining  $R_{TH}$  is changed

- Norton Equivalent
  - Norton equivalent consists of a Norton current source in parallel with a Norton resistor
  - It's a dual of Thevenin equivalent circuit, and one can be derived from the other
  - It can be deduced from the source transform

$$\boxed{i_{nor} = \frac{V_{TH}}{R_{TH}} \quad R_{TH} = R_{nor}}$$

- Determining  $R_{TH}$ 
  - In a circuit with ideal voltage and/or current source<sup>1</sup>
  - Replace the voltage source with a short and a current source with an open
  - Find the equivalent resistance across  $a$  and  $b$  using resistor transform

---

<sup>1</sup>Note: This technique does not apply when there are dependent sources in the circuit