

First Order Time-Dependent Circuits

Michael Brodskiy

Professor: N. Sun

February 22, 2023

- Natural Response

- An inductor or a capacitor can store energy when charge by current or a voltage source
- If they are abruptly disconnected, they will lose energy through a resistor
- The timing response of the circuit is called the natural response

- Time Constant

- Notice the equation

$$i(t) = I_0 e^{\frac{-Rt}{L}}$$

- The term $\frac{L}{R}$ is called the time constant of the circuit
- The equation can be changed to:

$$i(t) = I_0 e^{-\frac{t}{\tau}}$$

- Time constant is represented as τ and is the time it takes for the current to reduce to 37% of original value
- When we say long time, we typically mean 5 or more time constants
- Momentary events such as opening of the switch and circuit response that follows is called transient response
- The response of the circuit after a long time (several time constants) is called the steady-state response

- Step Response of an RL Circuit

- Step response of a circuit is the timing response when you suddenly apply a voltage or current source across resistor
- Applying KVL, the differential equation comes out to be:

$$-V_s + iR + L \frac{di}{dt} = 0$$

- Solving this, we obtain:

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-\frac{R}{L}t}$$

- RC Circuit

- The differential equation for an RC Circuit is:

$$-I_s + \frac{v}{R} + C \frac{dv}{dt} = 0$$

- Solving this equation, we get:

$$I_s R + (V_0 - I_s R) e^{-\frac{t}{RC}}$$