

# Electrocardiogram Circuits & Signals EECE2150

Michael BRODSKIY

April 20, 2023

|                 |                                 |
|-----------------|---------------------------------|
| Date Performed: | April 6, 2023                   |
| Partner:        | Juan ZAPATA, Oluwalaanu ADEBOYE |
| Instructor:     | Professor SUN                   |

## 0 Introduction

The purpose of this laboratory experimentation was to unify all of the course concepts. Through integration of rudimentary circuit components like resistors, capacitors and inductors, in tandem with more complex components like operational amplifiers and band-pass filters, the goal was to construct a circuit that, when connected to three electrodes on the body, would generate a filtered electrocardiogram signal. Additionally, an analog-to-digital converter was then used to generate a heart rate plot from a sample.

## 1 Discussion and Analysis

## 2 Conclusion

Overall, this laboratory experiment allowed for an adequate unification of course concepts. By reiterating the basics and strengthening more advanced and, thus, difficult concepts, the lab creates a stronger understanding of all critical course concepts.