

First Order Time-Dependent Circuits

Michael Brodskiy

Professor: N. Sun

February 15, 2023

- Natural Response

- An inductor or a capacitor can store energy when charge by current or a voltage source
- If they are abruptly disconnected, they will lose energy through a resistor
- The timing response of the circuit is called the natural response

- Time Constant

- Notice the equation

$$i(t) = I_0 e^{\frac{-Rt}{L}}$$

- The term $\frac{L}{R}$ is called the time constant of the circuit
- The equation can be changed to:

$$i(t) = I_0 e^{-\frac{t}{\tau}}$$

- Time constant is represented as τ and is the time it takes for the current to reduce to 37% of original value
- When we say long time, we typically mean 5 or more time constants
- Momentary events such as opening of the switch and circuit response that follows is called transient response
- The response of the circuit after a long time (several time constants) is called the steady-state response