

Thevenin and Norton Equivalents

Michael Brodskiy

Professor: N. Sun

January 30, 2023

- Circuit Equivalence
 - If there are two circuits, and the same voltage, v_a is applied to both, if $I_A = I_B$ then the circuits are considered equivalent
 - Same thing for same current applied and same voltage output
- Resistor Equivalence
 - Resistors can be connected in circuits like a delta connection
 - As well as a Y connection
 - A delta connection can be transformed into a Y connection and vice versa using transformation technique
 - This will often help in circuits
- Transformations can be established from one to the other, as shown in Figure 1, using the following

$$\boxed{R_1 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_c R_a}{R_a + R_b + R_c}, \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}}$$

$$\boxed{R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}, \quad R_2 = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}, \quad R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}}$$

- A voltage source with a series resistor can be transformed into a current source with a resistor in parallel, as shown in Figure 2
- A parallel resistor with a voltage source can be removed (replaced by an open) for transformation, as shown in Figure 3
- A series resistor with a current source can be removed (replaced by a short) for transformation, as shown in Figure 4

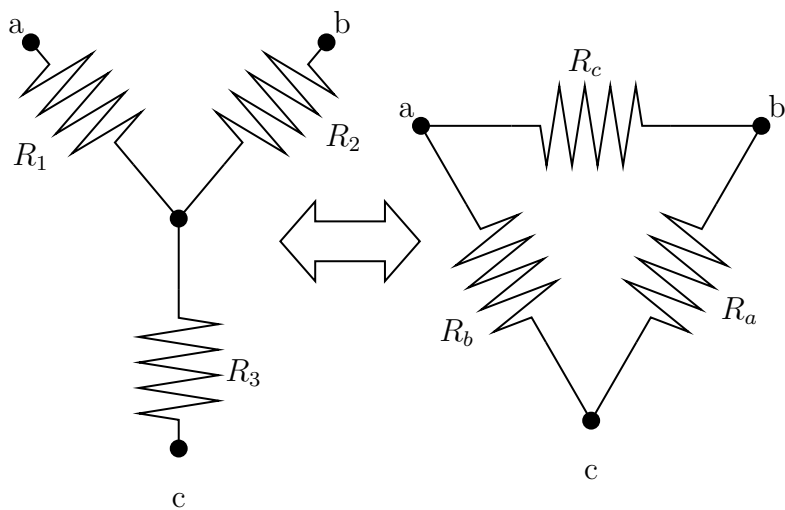


Figure 1: Delta and Y Circuit Configurations

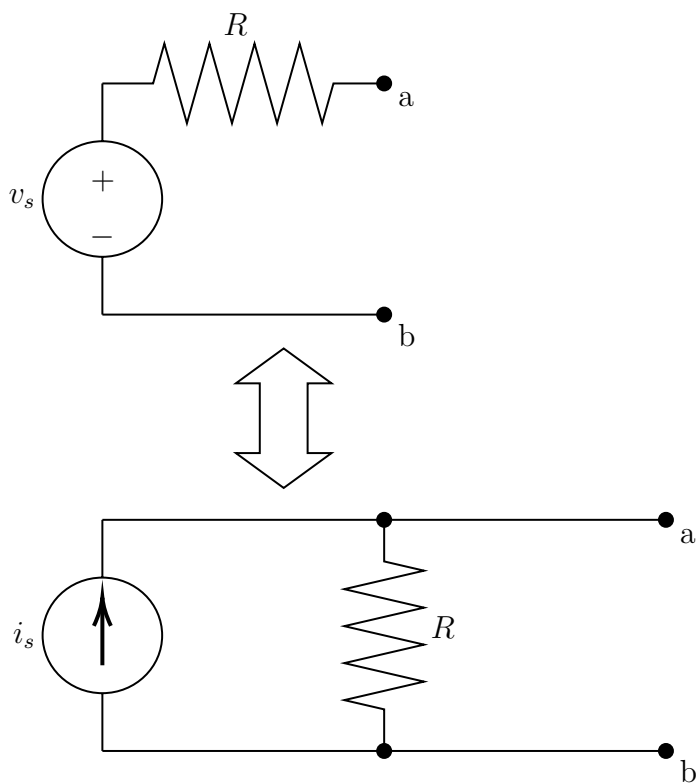


Figure 2: Converting Between Voltage and Current

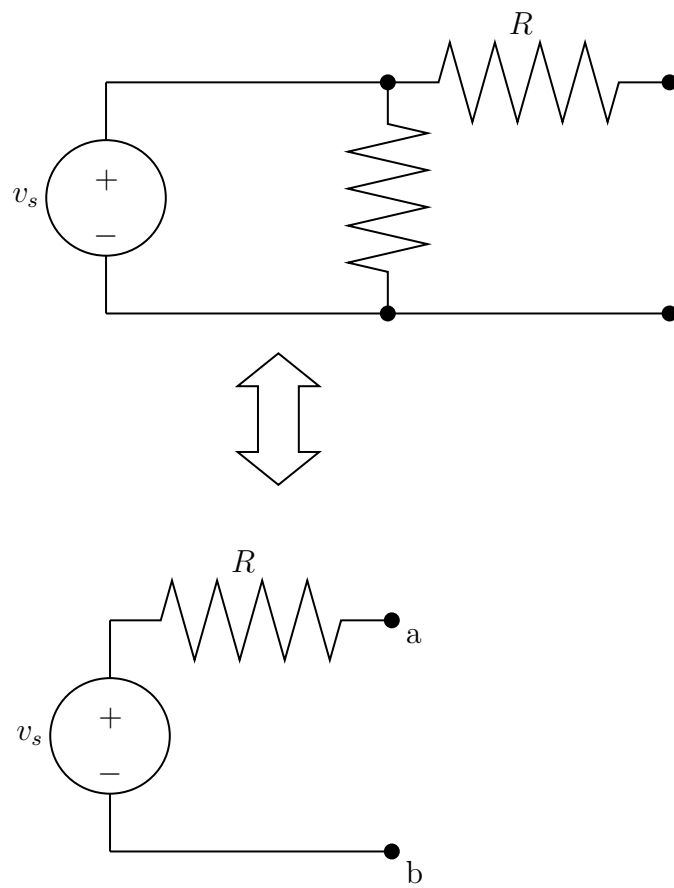


Figure 3: Converting Voltage Sources

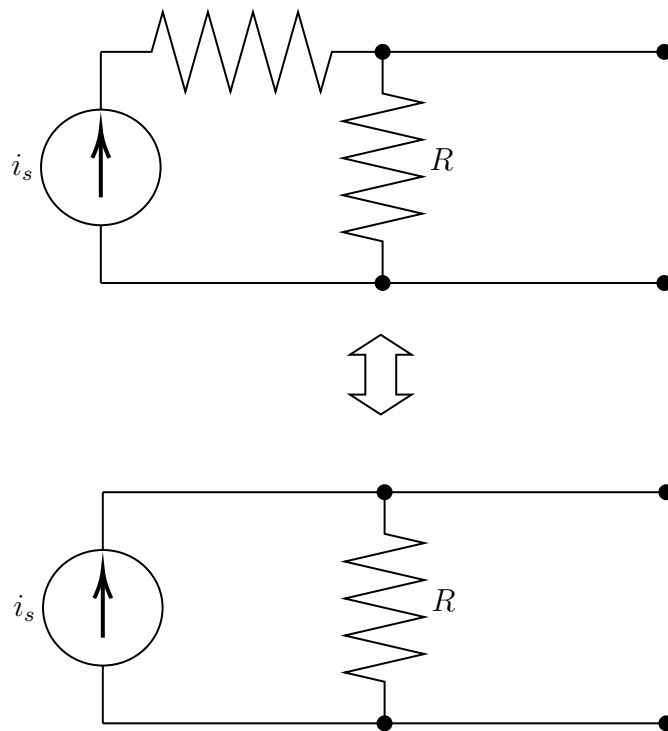


Figure 4: Converting Current Sources

- Some systems may be very complex, but we may be only interested in how it behaves at two terminals
 - Actual circuit can be converted into an equivalent circuit, called Thevenin equivalent
 - It essentially replaces the actual circuit with a voltage source with a series resistor
 - The voltage source is called the Thevenin voltage V_{TH}
 - The equivalent input resistance is called the Thevenin resistor R_{TH}
- Thevenin Equivalence is a two-step process:
 1. Analyze the circuit and find the open circuit voltage v_{oc}
 2. Analyze the circuit and find the short circuit current across the terminal i_{sc}
 - Some circuits only work properly over a certain range of loads (not with $R_L = 0$, for example)
 - For this type of circuit, to determine R_{TH} use an acceptable R_L and compute R_{TH} by using the voltage divider equation shown below

$$V_{RL} = V_{TH} \frac{R_L}{R_{TH} + R_L}$$

- Note that only the process of determining R_{TH} is changed